

NORMAL

R4 OPEN

REQ

REQ

IT

IT

IR1

ER1

IR1

ER1

IR2

ER2

IR2

ER2

IR3

ER3

IR3

ER3

IR4

ER4

IR4


ER4

IR1 = 0 IR2 = 0 IR3 = 0 IR4 = ↑ What is the malfunction?

REQ = 4.61 K Ω WHAT IS THE MALFUNCTION

How many volts will be measured across R1 if R3 were shorted?

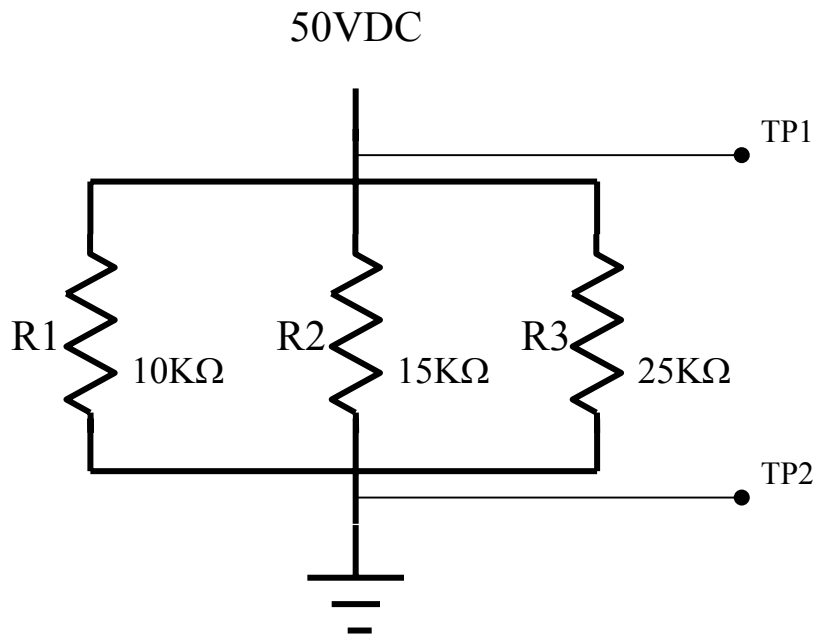How many volts will be measured across R1 if R3 were open?



NORMAL

REQ
IT
IR1
IR2
IR3
ER1

R1 OPEN

REQ
IT
IR1
IR2
IR3
ER1

R1 SHORT

REQ
IT
IR1
IR2
IR3
ER1

R3 IS OPEN. $R_T = \underline{\hspace{2cm}}$ $I_t = \underline{\hspace{2cm}}$

R2 is short $E_{r1} = \underline{\hspace{2cm}}$ $I_{R1} = \underline{\hspace{2cm}}$

Any open in a circuit makes the resistance $\underline{\hspace{2cm}}$ and the current $\underline{\hspace{2cm}}$

$R_{EQ} = 6K\Omega$ What is the malfunction?

$I_T = 7 \text{ mA}$ what is the malfunction?